

ECE 2300

Electronics Circuits and Electronics Devices Laboratory

Gregg Chapman


Laboratory 6

Diodes



Background

- Diodes
 - Small Signal
 - Rectifiers
 - Half wave
 - Full Wave
 - Zener Diodes
 - Light Emitting Diodes (LED)



Diodes

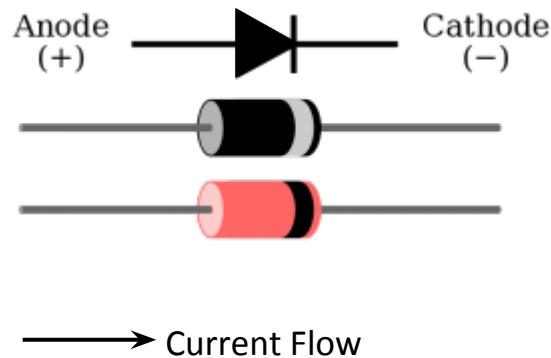


Zener Diodes

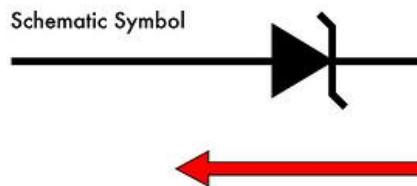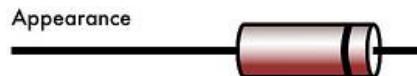

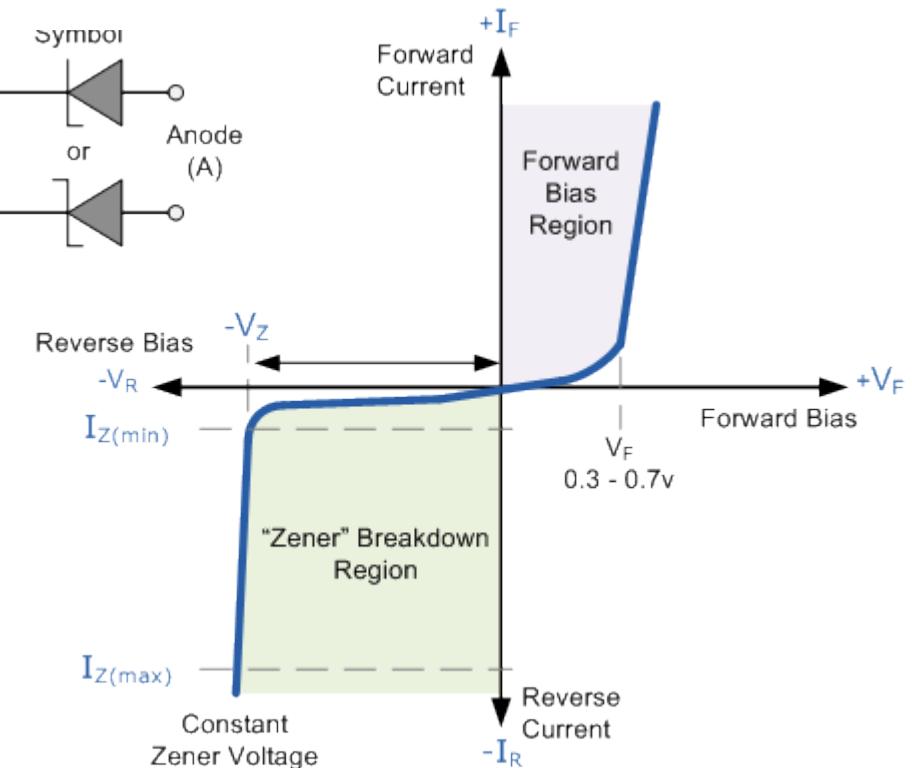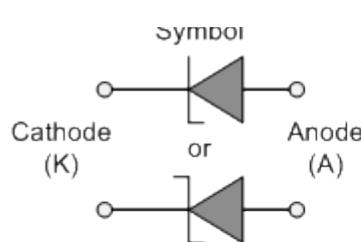Backwards current flow too, but only past the "zener" breakdown voltage



Light Emitting Diodes

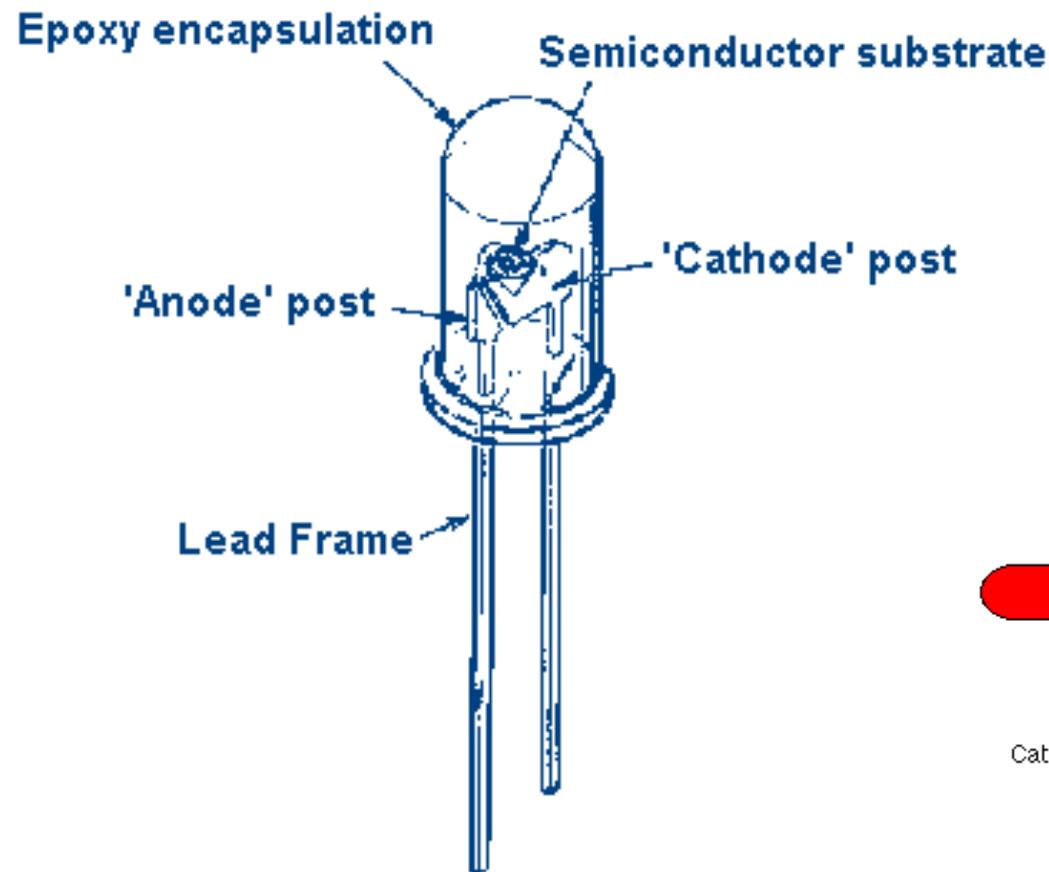

$$V_F = 2.2 \text{ V}$$

Lab Supplies

- Resistors

- 1 150 Ohm
- 1 1.00 Kohm
- 1 4.99 KOhm
- 1 10.0 Kohm

- Diodes

- 1 1N4001-T
- 4 1N4148G
- 2 1N5231BTR
- 1 WP3A8GD (Green LED)

- Transformer (From Lab Monitors)

- 1 PE-5156XNL

Lab Supplies

- Breadboard
- Oscilloscope
- Function Generator
- Power Supply
- BNC-to-Mini-grabber (2)
- BNC Cable
- BNC T-Adapter
- Banana to Mini-grabber, black (3)
- Banana to Mini-grabber, red (3)

Cabling



Test Set-up

- BNC T-Adapter on output of Function Generator
- BNC cable from T-Adapter to Channel 1 of the Oscilloscope
- BNC to Mini-clip from T-Adapter to the input
- BNC to Mini-clip from Channel 2 of the Oscilloscope to the output


Circuits

1. Half Wave Rectifiers (positive)
2. Half Wave Rectifier (negative)
3. Full Wave Rectifier
4. LED
5. Zener Diode
6. Zener Clipping Circuit

Function Generator Setup 1a

- Sine Wave
- Begin with 5V peak-to-peak amplitude
- Offset should remain at 0V
- Begin with 100 Hz


Half Wave Rectifier 1a

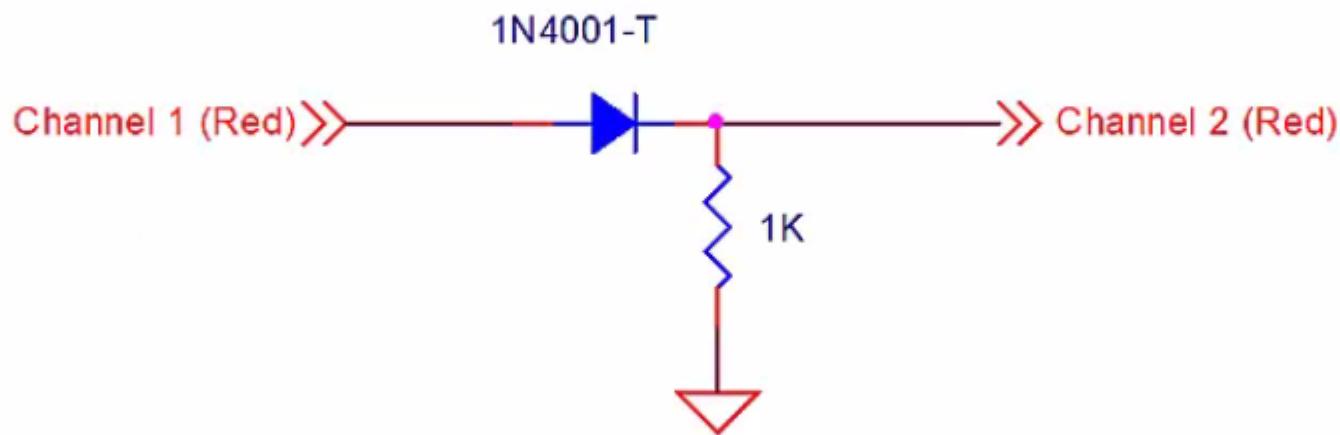


Function Generator Setup 1b & 2

- Sine Wave
- Begin with 5V peak-to-peak amplitude
- Offset should remain at 0V
- Change frequency to 100 Kilohertz

Half Wave Rectifier 1b

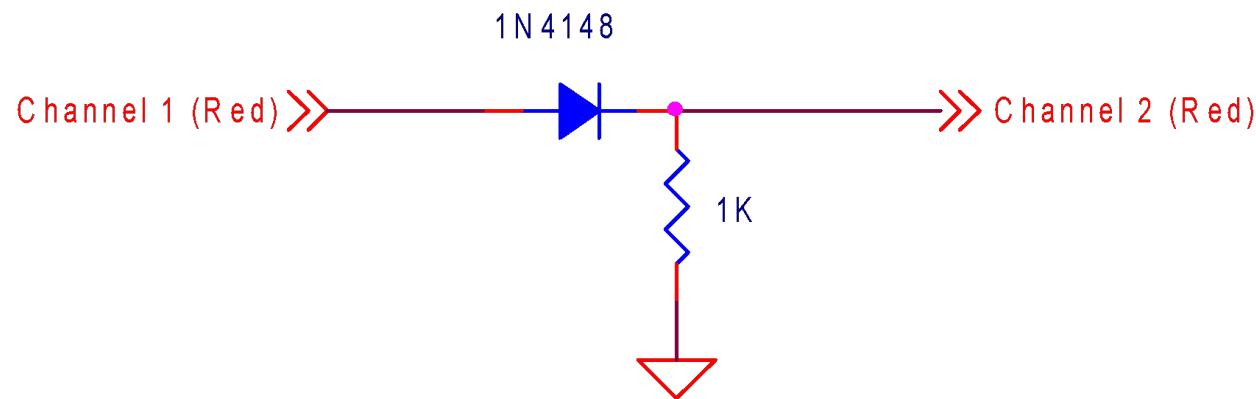

Half Wave Rectifier 2

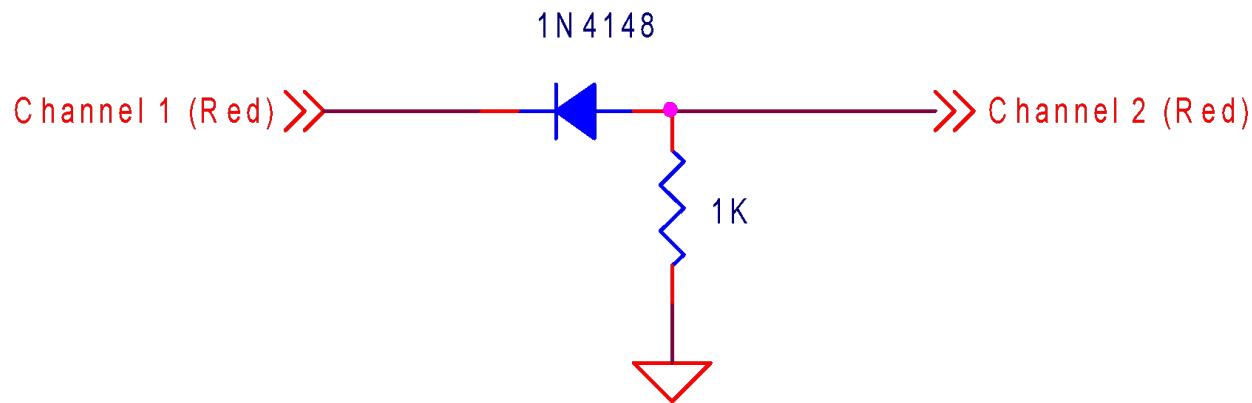


Measurements

- Circuits 1a ,1b and 2 (Half wave rectifiers):
 - Peak voltages (input, output and difference) at specified frequencies (100 HZ or 100 KHz. See table)

Function Generator Setup 3

- Sine Wave
- Begin with 5V peak-to-peak amplitude
- Offset should remain at 0V
- Change frequency to 10 Kilohertz

Full Wave Rectifier

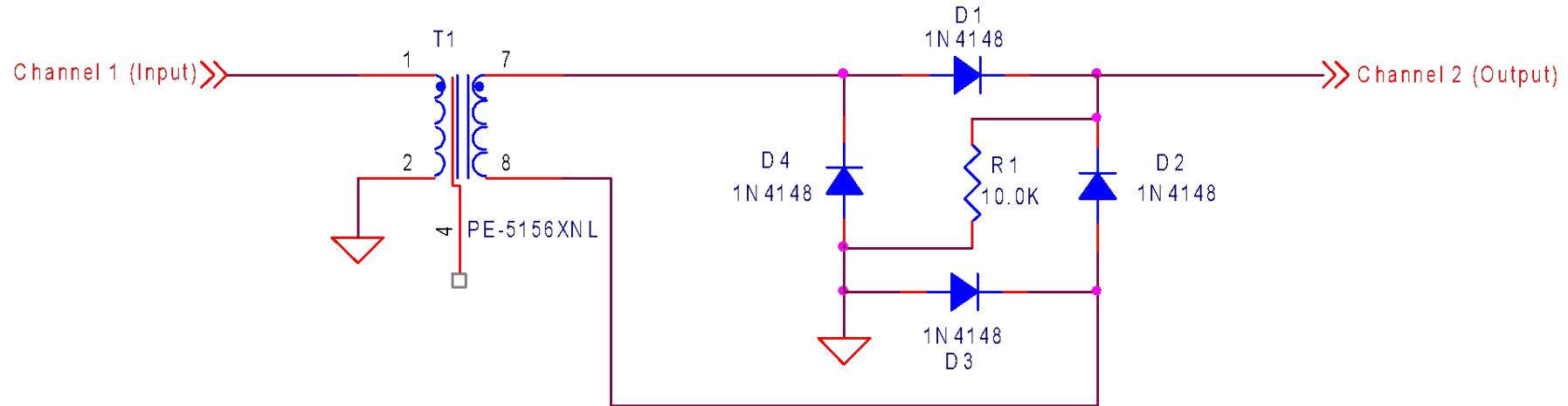

Measurements

- Circuits 1a ,1b and 2 (Half wave rectifiers):
 - Peak voltages (input, output and difference) at specified frequencies (100 HZ or 5 KHz. See table)
- Circuit 3 (Full Wave Rectifier)
 - Peak voltages (input, output and difference) at 10 KHz
 - Ripple voltage with 0.1 uF capacitor in parallel with 10 Kohm Resistor


Test Set-up

- +12V from Power Supply (+ output of dual section)
- Ground from Power supply (Black connector of dual section)
- Digital Multi-meter

Rigol DP1308A Triple Power Supply




LED Circuit

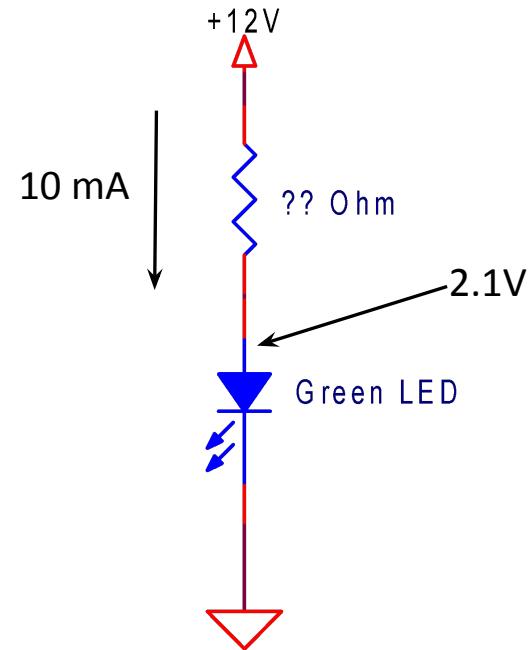

Calculations

- Circuit 4 (LED)
 - Calculate resistor required for 10mA in the LED. Assume 2.1V for voltage drop across LED. (Use closest resistor value available in kit for circuit).

Zener Diode

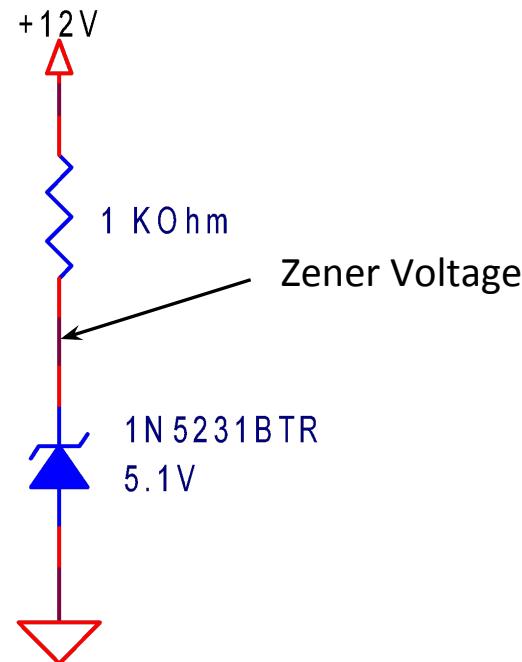


Measurements

- Circuits 1a ,1b and 2 (Half wave rectifiers):
 - Peak voltages (input, output and difference) at specified frequencies (100 HZ or 5 KHz. See table)
- Circuit 3 (Full Wave Rectifier)
 - Peak voltages (input, output and difference) at 10 KHz
 - Ripple voltage with 0.1 uF capacitor in parallel with 10 Kohm Resistor
- Circuit 4 (LED)
 - Measure current through LED
- Circuit 5 (Zener diode)
 - Measure current and voltage across Zener for resistor values of 150, 1.00K and 4.99 K Ohms.

Function Generator Setup 6

- Sine Wave
- 20V peak-to-peak amplitude
- 1000 Hz

Zener Input Clipping

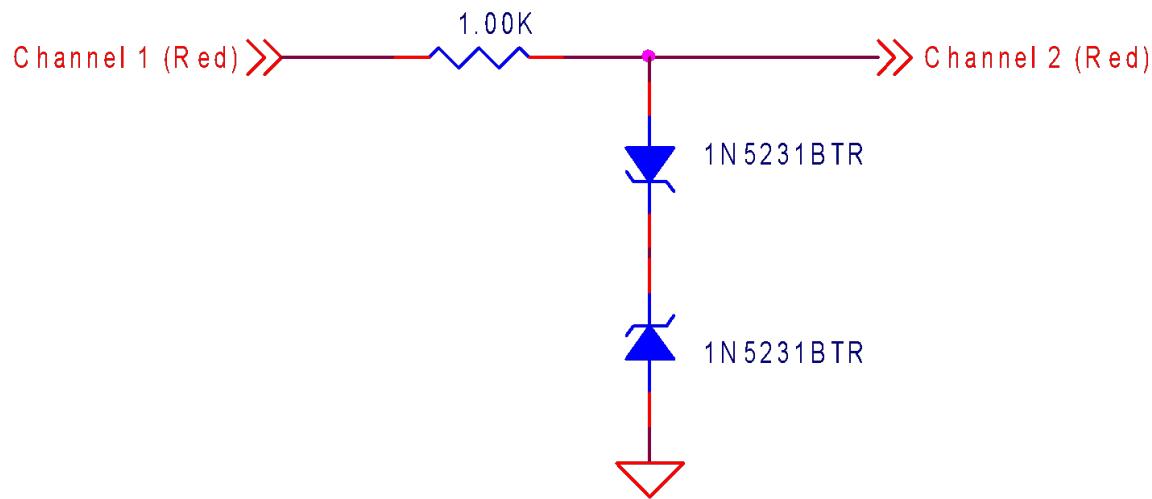


Measurements


- Circuits 1a ,1b and 2 (Half wave rectifiers):
 - Peak voltages (input, output and difference) at specified frequencies (100 HZ or 5 KHz. See table)
- Circuit 3 (Full Wave Rectifier)
 - Peak voltages (input, output and difference) at 10 KHz
 - Ripple voltage with 0.1 uF capacitor in parallel with 10 Kohm Resistor
- Circuit 4 (LED)
 - Measure current through LED
- Circuit 5 (Zener diode)
 - Measure current and voltage across Zener for resistor values of 150, 1.00K and 4.99 K Ohms.
- Circuit 6 (Zener clipping circuit)
 - Measure maximum positive voltage and minimum negative voltage.

Lab 6 Circuit Schematics


1a

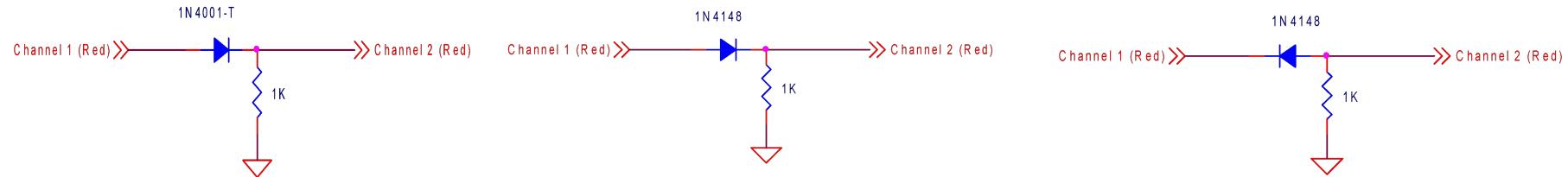


1b

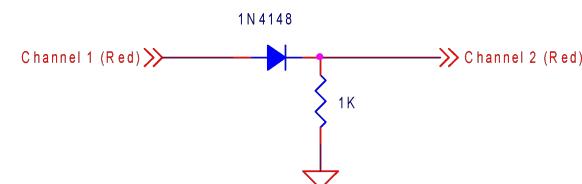


2

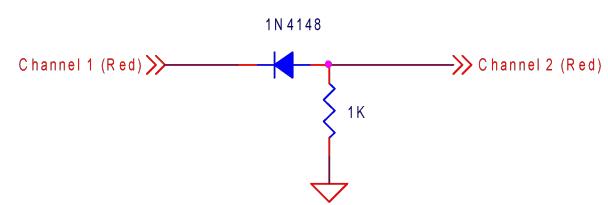


3

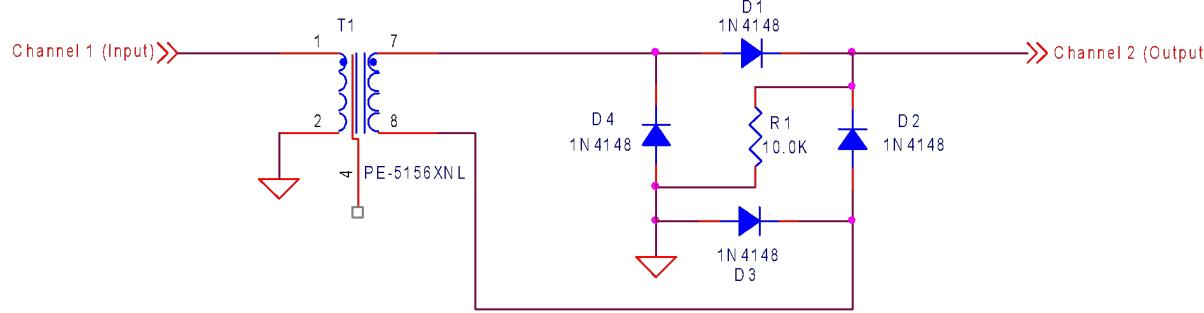

4

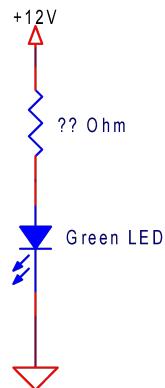


5

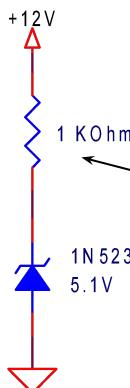

Three different values

6

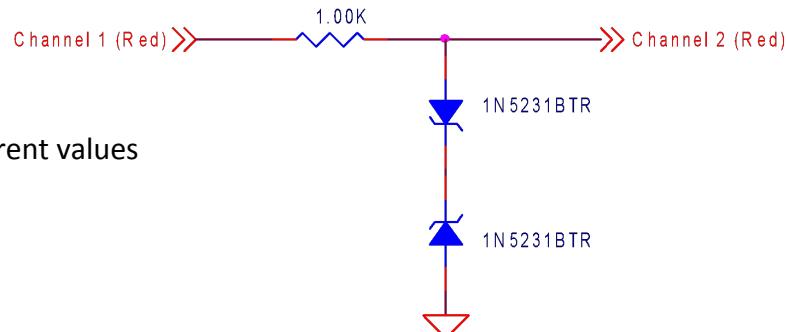

Lab 6 Results

Rectifiers

Circuit	Test Frequency	Peak Voltage In	Peak Voltage Out	Voltage Difference
Half Wave Rectifier 1a	100 Hz			
Half Wave Rectifier 1b	10 KHz			
Half Wave Rectifier 2	10 KHz			
Full Wave Rectifier	10 KHz			

Circuit	Ripple (millivolts)
Full Wave Rectifier with 0.1 uF Capacitor	

Zener Diode Results

Resistor Value	Measured Current	Zener Voltage
150 Ohm		
1.00 KOhms		
4.99 KOhms		

Zener Clipping Results

Saturation Voltage	Volts
Positive	
Negative	

LED Circuit

Calculated Resistor (Ohms)	Current (mA)